
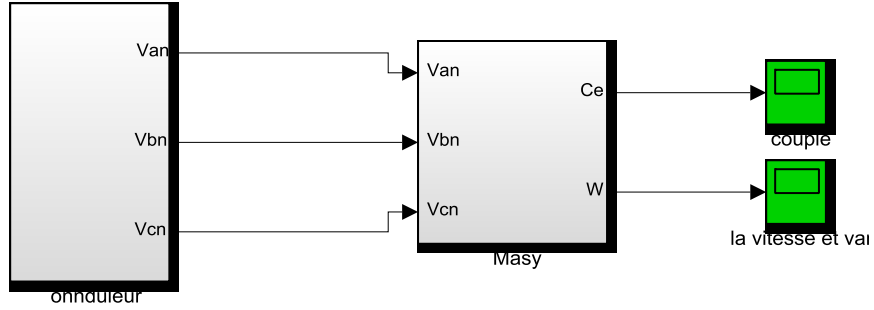



العمل التطبيقي الرابع

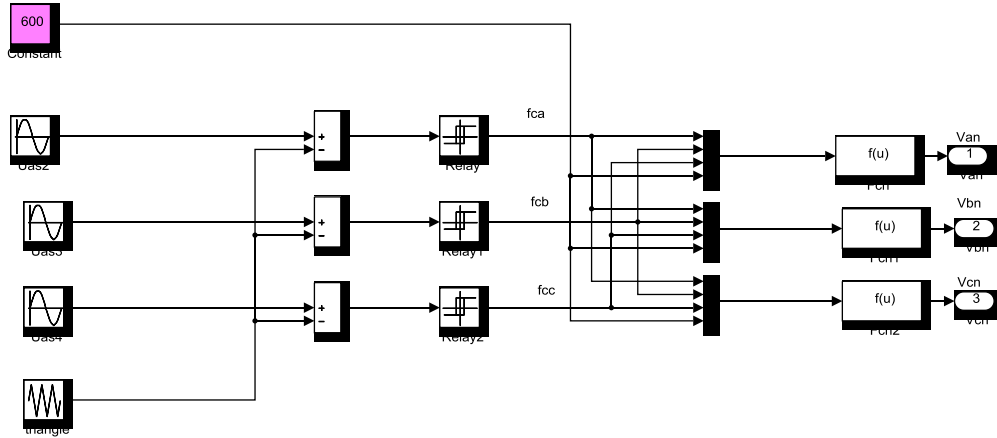

الشكل الاول



الشكل الثاني

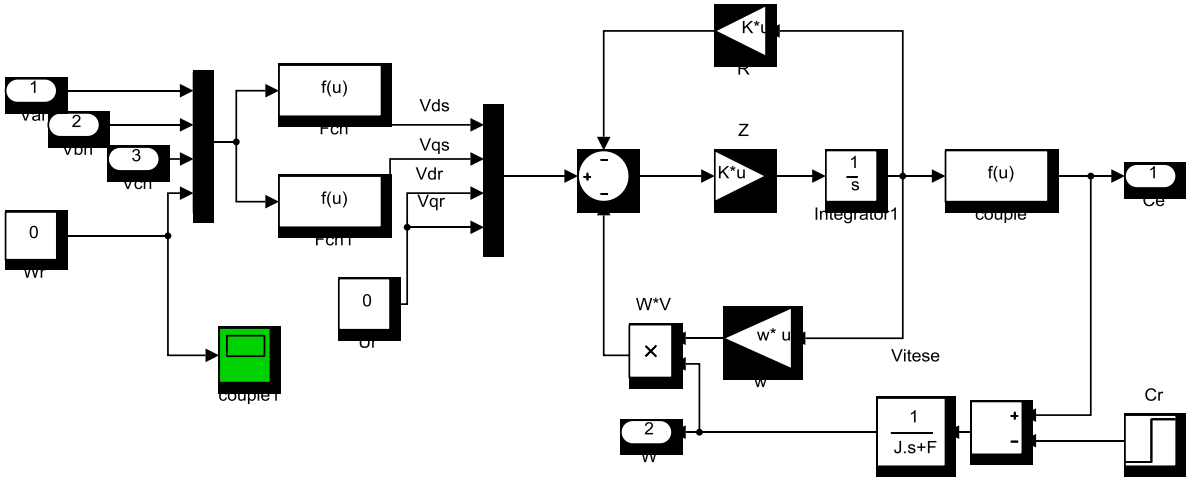

الشكل الثالث

Onduleur

Source Triangle

Case 1 : $[0 \ (1/f_s)/4 \ (1/f_s)*(3/4) \ 1/f_s]$

Case 2: $[0 \ 1 \ -1 \ 0]$

Les fonctions d'onduleurs

$$F_{cn} : (u[4]/3)*((2*u[1])-u[2]-u[3])$$

$$F_{cn1} : (u[4]/3)*(-u[1]+(2*u[2])-u[3])$$

$$F_{cn2} : (u[4]/3)*(-u[1]-u[2]+2*u[3])$$

Machine asynchrone

$$F_{cn} : \sqrt{2/3}*(u(1)*\cos(u(4))+u(2)*\cos(u(4)+2*\pi/3)+u(3)*\cos(u(4)+4*\pi/3))$$

$$F_{cn1} : -\sqrt{2/3}*(u(1)*\sin(u(4))+u(2)*\sin(u(4)+2*\pi/3)+u(3)*\sin(u(4)+4*\pi/3))$$

$$\text{Couple} : P*(M/Lr)*(3/2)*(u[3]*u[2]-u[1]*u[4])$$

Cr = step time 1 ; initial value 0; finale value = 15;

Les paramètres

```
clear;
clc;
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%paramètre de la machine asynchrone
Ls=0.274 ;
Lr=0.274 ;
Rr=3.805 ;
Rs=4.85 ;
M=0.258 ;
J=0.031 ;
P=1 ;
p=P ;
F=0 ;
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%paramètre de filtre
R=10 ;
L=100e-3 ;
C=250e-6 ;
A=L*C ;
B=L/R ;
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%% fréquence de la source triangulaire
fs=2000;
R=[Rs 0 0 0 ;
  0 Rs 0 0 ;
  0 0 Rr 0 ;
  0 0 0 Rr];
w=[0 0 0 0 ;
  0 0 0 0 ;
  0 M 0 Lr ;
  -M 0 -Lr 0];
L=[Ls 0 M 0 ;
  0 Ls 0 M ;
  M 0 Lr 0 ;
  0 M 0 Lr];
Z=inv(L);
```